

一、填空题

1.  $2\Omega$ ;  $16\text{V}$
2.  $4\text{H}$
3.  $2\text{A}$
4.  $0.02\text{H}$ ;  $50$
5.  $0.4\text{mJ}$
6.  $5\text{V}$

二、计算题

1.  $u_1 = -2\text{V}, u_2 = 7\text{V}$

2.  $\dot{I}_1 = (4 + j3)\text{A}, \dot{I}_2 = (4 + j1)\text{A}, \dot{I}_3 = j1\text{A}$

3.  $u_C(t) = (12 - 6e^{-10t})\text{V}, t \geq 0;$

$$i_1(t) = (2 - 0.6e^{-10t})\text{A}, t > 0$$

4. (1) 
$$\begin{cases} U_1 = 3I_1 + 5I_2 \\ U_2 = -6I_1 - 4I_2 \end{cases}$$

(2)  $\Pi$ 形等效电路略;  $Y_1 = -\frac{1}{2}\text{S}; Y_2 = -\frac{1}{9}\text{S}; Y_3 = \frac{5}{18}\text{S}; g = \frac{11}{18}\text{S}$

5.  $R = 2000\Omega, L = 1\text{mH}$ 时:  $P_{\max} = 5\text{mW}$

6.  $u_1(t) = 31.5\sqrt{2}\cos(t - 8.7^\circ)\text{V}$